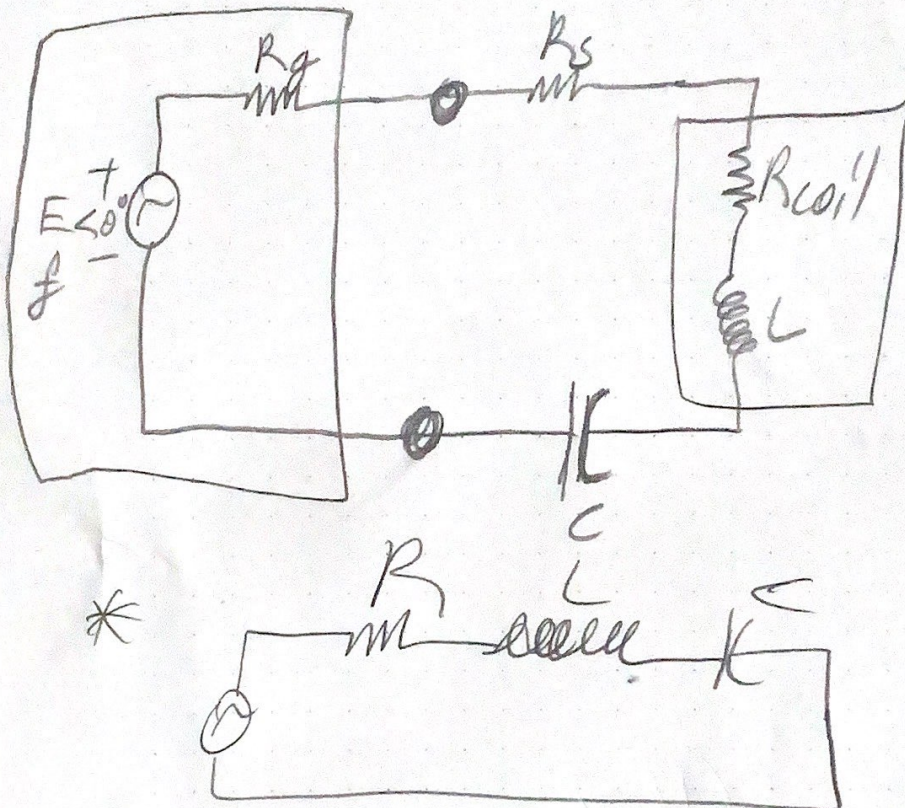


Resonance

It is one of the most important circuit used in electronic.

1- Series Resonant Circuit

2- Parallel Resonant Circuit



$$R = R_g + R_s + R_{coil}$$

$$Z_T = R + jX_L - jX_C$$

$$= R + j(X_L - X_C)$$

* Z_T is purely resistive. Inductor and capacitor cancel each other.

$$\boxed{Z_T = R}$$

thus,

$$\frac{WL}{X_L} = \frac{1}{\frac{WC}{X_C}}$$

$$\star \boxed{W_S = \frac{1}{\sqrt{LC}}} \text{ (rad/s)}$$


$$W = 2\pi f$$

$$\frac{1}{\sqrt{LC}} = 2\pi f$$


$$\star \boxed{f_S = \frac{1}{2\pi\sqrt{LC}}} \text{ (Hz)}$$

* At resonance ~~total~~ ^{phase} current in the circuit
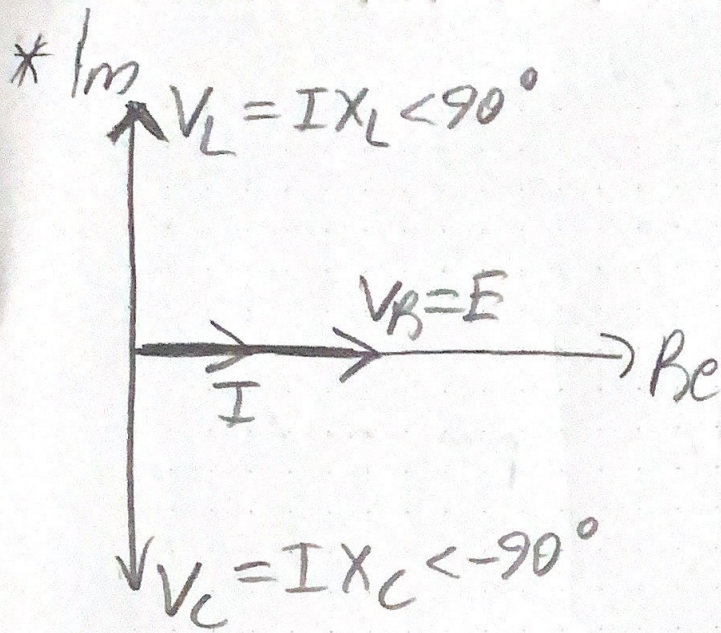
$$I = \frac{E}{Z_T} = \frac{E \angle 0^\circ}{R \angle 0^\circ} = \frac{E}{R} \angle 0^\circ$$



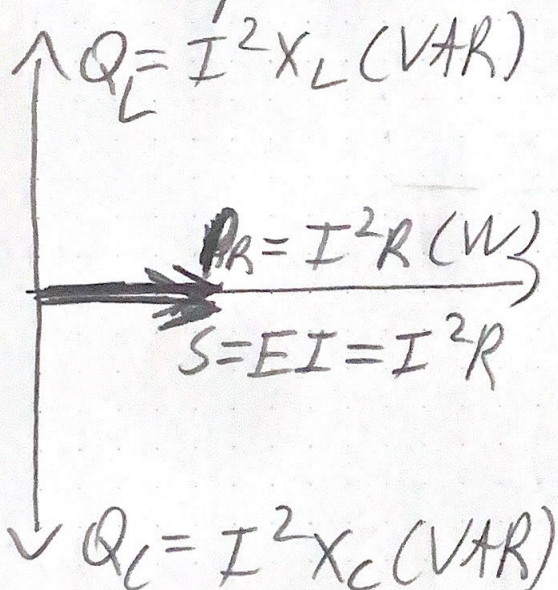* Let's determine average power and reactive powers



* Quality Factor;

$$Q = \frac{\text{reactive power}}{\text{active power}} \Rightarrow Q_s = \frac{I^2 \widetilde{X_L}}{I^2 R} \xrightarrow{\text{important}} \boxed{\frac{WL}{R}}$$

Quality factor

$www.onada.com.tr$

* If inductor has coil

$$Q_{\text{coil}} = \frac{X_L}{R_{\text{coil}}}$$

$$* Q_S = \frac{\frac{V_L}{I} X_L}{\frac{I R}{E}} = \frac{V_L}{E}$$

$$V_C = V_L = Q_S E \quad \text{! at "resonance"}$$

Impedance of a Series Resonant Circuit

$$\begin{aligned} * Z_T &= R + j\omega L - \frac{j}{\omega C} \\ &= R + j \left(\omega L - \frac{1}{\omega C} \right) \\ &\quad \left(\frac{\omega^2 LC - 1}{\omega C} \right) \end{aligned}$$

$$Z_T = \sqrt{R^2 + \left(\frac{\omega^2 L C - 1}{\omega C} \right)^2}$$

$$\theta = \tan^{-1} \left(\frac{\omega^2 L C - 1}{\omega R C} \right)$$

1- When $\omega = \omega_s$

$$Z_T = R$$



$$\theta = \tan^{-1} 0 = 0$$

2- When $\omega < \omega_s$

capacitor behaves like open circuit in DC. ★ To sum up, impedance must appear CAPACITIVE in this region


3- When $\omega > \omega_s$

Impedance must be inductive.

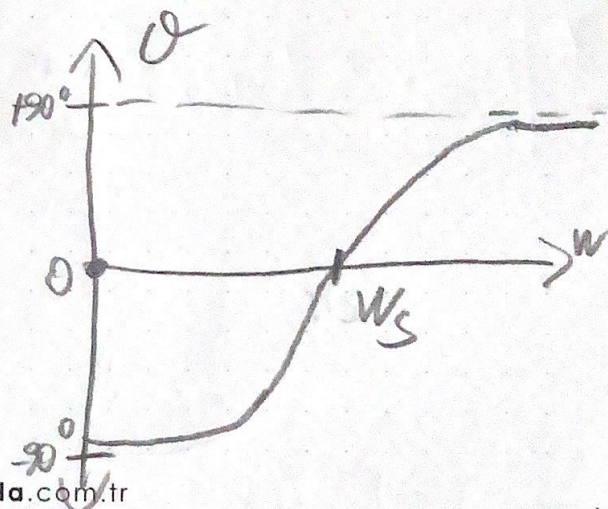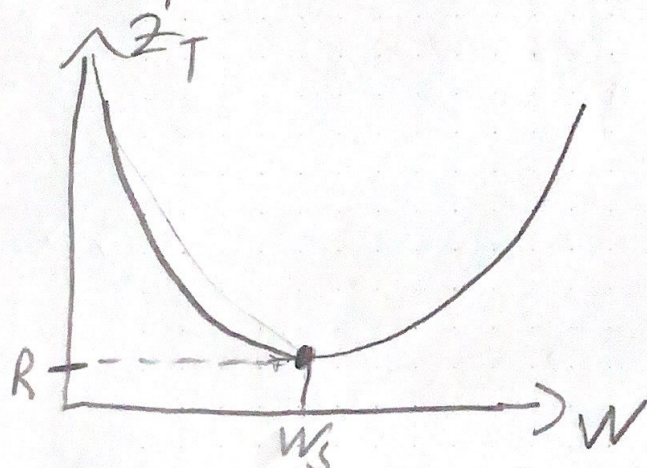

Power, Bandwidth and Selectivity of a Series Resonant Circuit.
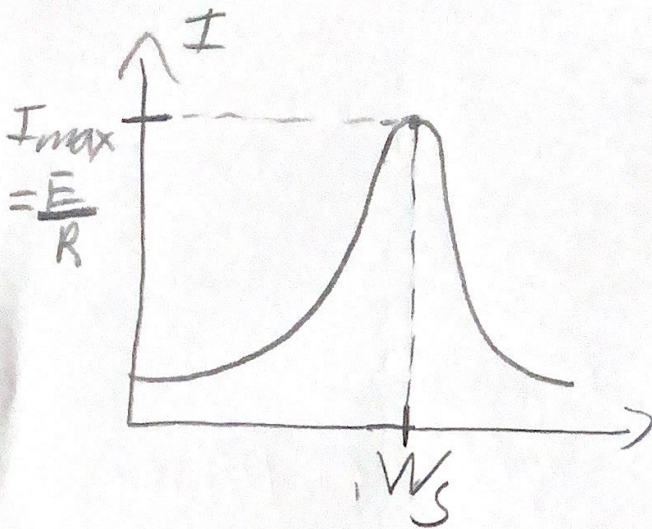
$$I_{\max} = \frac{E}{R} \} \text{ at resonance}$$




* total power at any frequency

$$P = I^2 \cdot R$$

$$* P_{\max} = I_{\max}^2 R = \frac{E^2}{R} \text{ at resonance}$$

Selectivity Curve

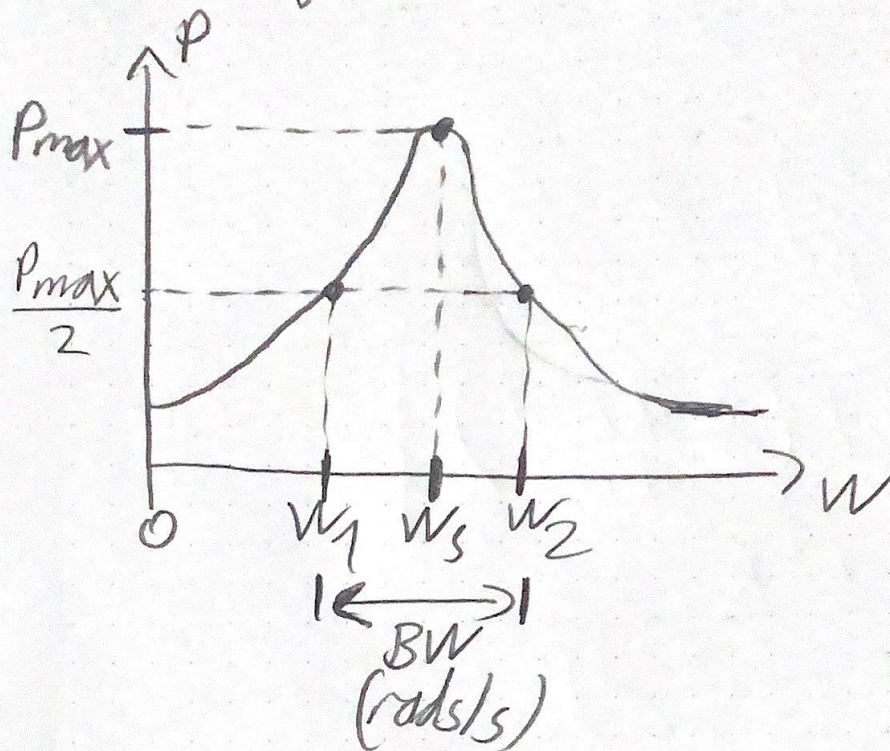

-if BW very narrow, circuit have high selectivity. Otherwise, if it's large have low selectivity

power at any frequency,

$$P = I^2 R$$

$$P = \left(\frac{E}{Z_T} \right)^2 \cdot R$$

$$\left[R + j \left(\frac{\omega^2 L C - 1}{\omega C} \right) \right]^2$$

$$P = \frac{E^2 R}{R^2 + \left(\frac{\omega^2 L C - 1}{\omega C} \right)^2}$$

* half power frequencies, the power must be

$$P_{hpf} = \frac{E^2}{2R}$$

$$I_{hpf} = \sqrt{\frac{P_{hpf}}{R}} = \sqrt{\frac{E^2}{2R^2}} = \sqrt{\frac{I_{max}^2}{2}}$$

$I_{max} = \frac{E}{R}$

$$I_{hpf} = \frac{I_{max}}{\sqrt{2}}$$

$$* \boxed{\omega^2 LC - 1 = \omega RC \text{ (at half power)}}$$

$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

Önemli

$$* BW = \omega_2 - \omega_1$$


$$\boxed{BW = \frac{R}{L} \text{ (rad/s)}}$$

$$BW = \frac{\omega_s R}{\omega_s L} = \frac{\omega_s}{Q_s} \text{ (rad/s)}$$

$$* BW = \frac{f_s}{Q_s} \quad (Hz)$$

Parallel Resonance


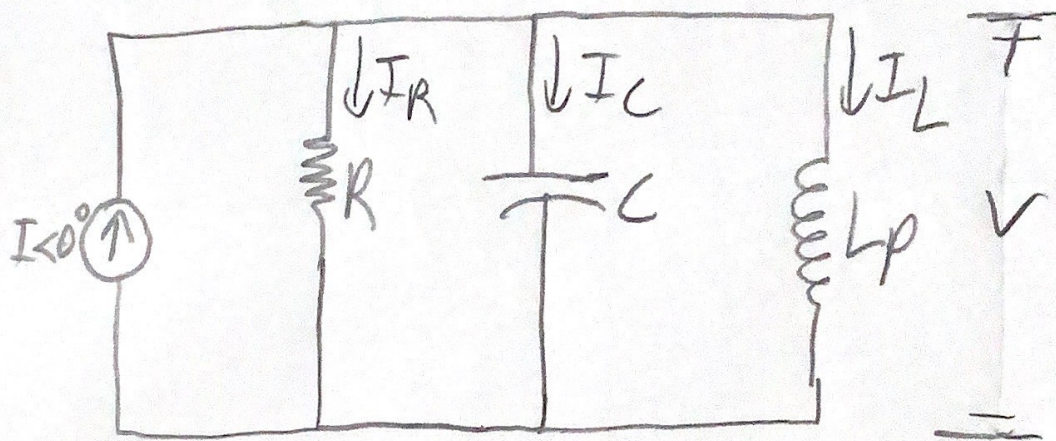
best analyzed using a constant current source.



$$* W_p = \frac{1}{\sqrt{LC}} \sqrt{1 - \frac{R_{coil}^2 \cdot C}{L}}$$

Önemli:
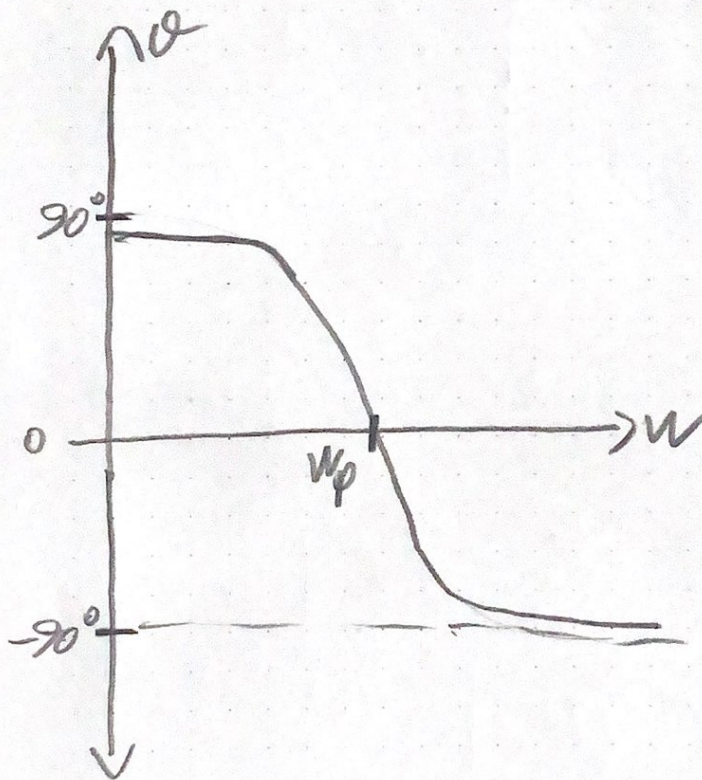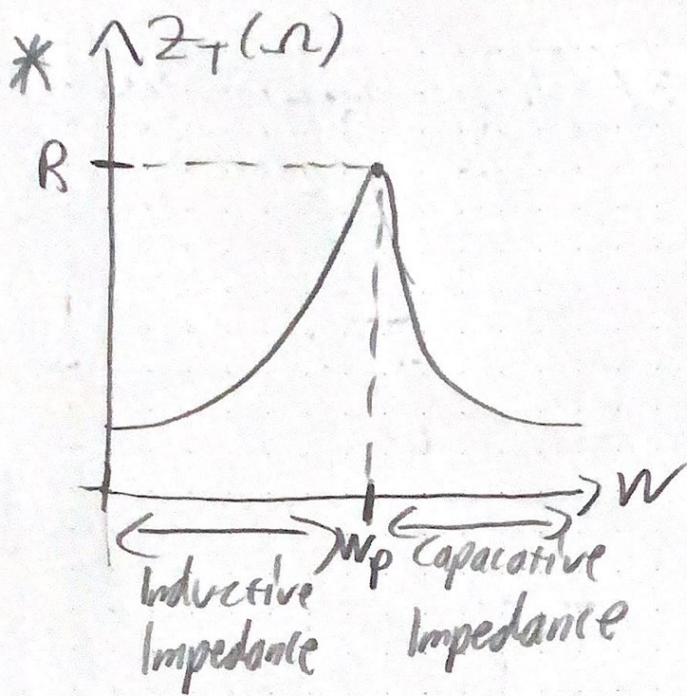
$$* W_p \cong \frac{1}{\sqrt{LC}}, \quad \text{for } L/C \geq 100 R_{coil}$$



$$\star Q_p = \frac{\text{reactive power}}{\text{average power}}$$

$$= \frac{V^2/X_L}{V^2/R}$$

$$\star I_R = \frac{V}{R} = I$$

$$\star I_L = \frac{V}{X_L \angle 90^\circ}$$

$$= \frac{V}{R/Q_p} \angle -90^\circ$$

$$= Q_p I \angle -90^\circ$$

$$\star I_C = \frac{V}{X_C \angle -90^\circ}$$

$$= \frac{V}{R/Q_p} \angle 90^\circ$$

$$= Q_p I \angle 90^\circ$$

★ Half power frequencies,

$$\star \omega_1 = \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}} \text{ (rad/s)}$$

$$\star \omega_2 = \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$\star BW = \omega_1 - \omega_2 = \frac{1}{RC} \text{ (rad/s)}$$

$$\star BW = \frac{\omega_p}{Q_p} \text{ (rad/s)}$$